

# Application Note

## Keep the Balance – Balancing of Supercapacitors



ANP090 // RENÉ KALBITZ

### 1 Introduction

Supercapacitors (SC) usually operate at low voltages of around 2.7 V. In order to reach higher operating voltages, it is necessary to build a cascade of serial connected SC cells. <sup>[1] [2]</sup> Due to production or aging related variations in capacitance and insulation resistance the voltage drop over individual capacitors may exceed the rated voltage limit. Thus, a balancing system is required to avoid accelerated aging of the capacitor cell. <sup>[3] [4]</sup> In the following, we want to explain the effect of unequal voltage division in such cascades in principle. To improve the understandability we consider a series stack of two capacitors.<sup>1</sup> In this note, we review the theoretical background and we provide some measurements as well as discussions on practical examples. The goal is to provide an overview on possible balancing strategies as well as an understanding of the explained concepts. The developer is invited to choose and adapt any strategy to meet specific requirements. For further information concerning the design-in process, please read our application note [ANP077<sup>\[5\]</sup>](#) “Supercapacitor – A Guide for the Design-In Process”

### 2 Imbalance of Serial Connected Supercapacitors

A capacitor may be modeled by a parallel connection of an R-C unit and a insulation resistance. For the moment we neglect the insulation resistance and consider a series stack of two capacitors with capacities  $C_1$  and  $C_2$ . The conserved quantity in such a stack is the condensed charge  $q$  at the capacitor, i.e. at its internal interfaces. Using the conservation of charge  $V_{1,2} = q/C_{1,2}$  the voltage drop over each capacitor is

$$V_1 = \frac{V_g}{\left(\frac{C_1}{C_2} + 1\right)}$$

and

$$V_2 = \frac{V_g}{\left(\frac{C_2}{C_1} + 1\right)}$$

with  $V_g = V_1 + V_2$  as the total voltage. (For more detail see also A.1) If both capacitance values are equal, the voltage at the terminals of two serial connected capacitors is equally

$$V_1 = V_2 = \frac{V_g}{2} = V_r$$

Thus, the system is balanced and each capacitor is charged at its rated voltage  $V_r$ .

In the following we may consider the case where  $C_1$  is larger than  $C_2$ . With above equations it can be shown (see A.1) that the voltage drop at each terminal is unequal by

$$\Delta V = \mp \frac{V_g}{2} \cdot \left| \frac{C_1 - C_2}{C_1 + C_2} \right|$$

With the voltage difference  $\Delta V$ , which is in the following referred to as imbalance, we may write

$$V_1 = \frac{V_g}{2} - \Delta V$$

and

$$V_2 = \frac{V_g}{2} + \Delta V$$

Using the definition of capacitance  $C = \Delta q / \Delta V$  with  $q$  as charges at the capacitor interface and  $V$  as voltage at the capacitor), the above equation may be rewritten as

$$V_1 = \frac{V_g}{2} - \frac{\Delta q}{C_1}$$

and

$$V_2 = \frac{V_g}{2} + \frac{\Delta q}{C_2}$$

In order to adjust the voltage of each capacitor to  $V_r = V_1 = V_2$  the charge has to be increased at capacitor 1 and decreased at capacitor 2 by the amount of  $\Delta q$ . Using the definition of electrical current ( $I = dq/dt$ ) the voltage may be written as

$$V_1 = \frac{V_g}{2} - I_1 \cdot \frac{\Delta t}{C_1}$$

and

$$V_2 = \frac{V_g}{2} + I_2 \cdot \frac{\Delta t}{C_2}$$

The current  $I_{1,2}$  is interpreted as the electrical current that has to flow for a time period  $\Delta t$  to equalize this system. The constant current that is required to equalize a voltage difference  $\Delta V$  in a given time period  $\Delta t$  is

$$I_{1,2} = \frac{\Delta V}{\Delta t} C_{1,2}$$


<sup>1</sup> Any system may be reduced to an equivalent circuit of two capacitors.

# Application Note

## Keep the Balance – Balancing of Supercapacitors



### 3 Balancing Current and Balancing Time

 

**Figure 1: Balancing currents in a capacitor stack.**

We may use above equations for the estimation of the current magnitude. In this example we used the full tolerance range of the capacitance, which is 40% (-10%/+30%). Hence, for  $C_r = 10 \text{ F}$  we obtain  $C_1 = 13 \text{ F}$  and  $C_2 = 9 \text{ F}$ . The total voltage of  $5.4 \text{ V}$  provides then a voltage difference  $\Delta V = 0.49 \text{ V}$  (i.e. at  $C_2$  the voltage drop is  $V_2 = 3.19 \text{ V}$  and at  $C_1$  the voltage drop is  $V_1 = 2.21 \text{ V}$ ). The  $\Delta V \approx 0.5 \text{ V}$  is the largest possible imbalance. To illustrate this situation, we use the circuit in Figure 1. The balancing current necessary to balance  $C_1$  and  $C_2$  within 1 sec respectively are:

$$I_1 = \frac{0.5 \text{ V}}{1 \text{ sec}} \cdot 13 \text{ F} = 6.5 \text{ A}$$

$$I_2 = \frac{0.5 \text{ V}}{1 \text{ sec}} \cdot 9 \text{ F} = 4.5 \text{ A}$$

Hence,  $C_1$  needs to be charged with  $I_1 = 6.5 \text{ A}$  and  $C_2$  needs to be discharged  $I_2 = 4.5 \text{ A}$ . The current that has to be provided by the balancing terminal can be calculated with Kirchhoff's current law. We may consider currents that flow out of the junction as negative and currents that flow into the junction as positive. Since  $I_1$  and  $I_2$  flow out of the junction and the balancing current  $I$  into the junction, the balancing current is

$$I = 11 \text{ A} = 6.5 \text{ A} + 4.5 \text{ A}$$

Although the result may vary depending on  $\Delta V$  and  $\Delta t$  this example of calculation may show that balancing at the characteristic RC-time requires currents of several amperes. The balancing current, required to balance a strongly imbalanced system of  $\Delta V = 0.5 \text{ V}$  (as calculated above) in within  $\Delta t$  can be estimated with

$$I = 2 \cdot \frac{0.5 \text{ V}}{\Delta t} \cdot C_r$$

So far we have neglected the insulation resistance, which starts to dominate the electrical behavior as soon as the SC is fully charged and the charging current becomes smaller than the leakage current  $I_{\text{leak}}$ . Most manufacturers specify a measurement time of 72 h at rated voltage  $V_r$  to determine  $I_{\text{leak}}$ . Under these conditions the capacitor may be simply modeled by an ohmic resistance  $R_{\text{iso}} = V_r / I_{\text{leak}}$ . Hence, if a capacitor is fully

charged a serial stack of SC may be considered as a stack of serial connected resistances, which constitute a voltage divider.

### 4 Balancing Strategies

The literature [3,4,6,7,8] categorizes balancing strategies by different properties like

- energy dissipative behavior,
- balancing speed,
- the type of technology that is used or
- pricing

Thus, when it comes to choosing the right balancing strategy, it is important to now all the parameters and constrains of the specific application to make the right choice.


In this note, we distinguish mainly between:

- active balancing and
- passive balancing

Active balancing involves the utilization of actively controlled switches or amplifying systems. [3,8] Passive balancing utilizes shunts or self-regulating resistors to lower the effect of overvoltage. Compared to passive balancing, active balancing may be fast, in some cases energy efficient but also relatively cost intensive. Passive balancing, on the contrary, is relatively slow, leads to reduction of the charge storing capabilities but it is more cost efficient than active balancing solutions.

#### 4.1 Passive Balancing with Resistors

Figure 2 presents an example of passive balancing with a resistor. The red and green arrows represent the corresponding physical current flow for the case were  $C_1$  has either over ( $+\Delta V$ ) or under voltage ( $-\Delta V$ ). The current for the balancing speed is adjusted (or restricted) by the resistance of the balancing resistors.

 

**Figure 2: Circuit for passive balancing with resistors.**

The balancing resistors have to meet three main requirements:

- The resistance should be as low as possible to allow a fast balancing. This will be beneficial for the lifetime.
- The resistance should be as high as possible to minimize losses and minimize the self-discharge.

# Application Note

## Keep the Balance – Balancing of Supercapacitors



- The accuracy of the resistors/shunt should be sufficient ( $\leq 1\%$ ) in order to provide an accurate reference.

Clearly, it is necessary to find an optimum between short balancing times and low self-discharge.

The balancing resistance would have to be the order of the equivalent series resistance  $R_{ESR}$ , to balance the supercaps within the characteristic RC-time. This is a theoretical consideration and not practical, since it would mean we permanently short-circuit the SC. A good rule of thumb is one tenth of the insulation resistance, i.e.

$$R_b = 0.1 \cdot \frac{V_r}{I_{leak}}$$

With  $V_r$  as rated voltage and  $I_{leak}$  as leakage current (both values are given in the data sheet of the SC). Due to its magnitude,  $R_b$  balances differences in insulation resistances.

The maximum current that can flow at  $\Delta V$  is  $I_{max} = \Delta V/R_b$ . The time to equalize a imbalance  $\Delta V$  up to 95 % can be calculated with

$$t_b = \ln \left( \frac{100 \%}{100 \% - 95 \%} \right) \cdot (R_b \cdot C_r)$$

which can be well approximated with  $t_b = 3 \cdot R_b \cdot C_r$  (as explained in A.2). The resulting balancing times, given in Table 1, are indeed in the range of days. With the given balancing resistances, the self-discharge rate per day is about 41 %. Thus, for many power applications the resistance may even be reduced, at the expense of charge storing abilities and balancing speed.

Capacitance (F)	$I_{leak}$ (mA)	$R_b = R_{iso}/10$ ( $\Omega$ )	$t_b$ (h)
3	0.008	33750	84
5	0.012	22500	94
7	0.020	13500	79
10	0.030	9000	75
15	0.060	4500	56
25	0.068	3971	83
50	0.105	2571	107

**Table 1: Summary of balancing resistances and corresponding balancing times.**


### 4.2 Passive Balancing with Zener Diodes

An improved balancing time can be achieved, if the resistor is replaced by a Zener Diode as indicated in Figure 3. The arrows again indicate the electrical current flow, in case of a imbalance. The Zener diodes constitutes a variable resistor or a voltage dependent switched resistor. Since the internal resistance is reduced at the breakdown voltage, it is

possible to drastically reduce the balancing time in comparison the linear resistor.

Diodes may also serve as general protection against reverse polarity. Especially for larger stacks, it can be advisable to place Zener diodes in parallel to metal oxide semiconductor field effect transistors (MOSFET).

The accuracy of the breakdown voltage is, compared to the accuracy of ohmic resistors, usually relatively low. In total the tolerances could be as high as around 10 %.

 

**Figure 3: Circuit for balancing with Zener diodes.**

Possible overvoltages could be still avoided by a reduction of working voltage. For operations at higher temperatures, it might also be necessary to consider the shift of breakdown voltage due to the temperature coefficient.

The strong voltage dependence of the reverse current makes it difficult to calculate the balancing time accurately.<sup>[8]</sup> The actual current characteristic of commercial Zener diodes are often not given in the datasheet.

It is however possible to roughly estimate the balancing time on the basis of the above expression for  $t_b$  (see section 4.1) A rough estimate can be made with the rated power dissipation of the Zener diode  $P_r$ , usually given in the datasheet. If the diode breakdown voltage is equal to actual operating voltage,  $V_R$  we may substitute  $R_b^* = V_r^2/P_r$  into above expression for  $t_b$  and obtain

$$t_b^* = 3 \cdot \left( \frac{V_r^2}{f \cdot P_r} \cdot C_r \right)$$

with  $f$  as correction factor.


Due to the strong voltage dependence of the reverse current, it may be necessary to adjust  $f$  from case to case to its effective value. Since the diode will most of the time operate well below its total power dissipation we suggest  $f = 1/10$ .

### 4.3 Passive Balancing with MOSFETs

Another type of balancing can be utilized with a MOSFET as given Figure 4. Similar to the Zener diode, the MOSFET constitutes a voltage driven switch or variable resistor.

# Application Note

## Keep the Balance – Balancing of Supercapacitors

 


**Figure 4: Circuit for balancing with MOSFET**

The arrows again indicate the electrical current flow, which is similar to the passive balancing in Figure 2. As soon as the voltage imbalance exceeds the threshold voltage of the MOSFET, the increased drain voltage leads effectively to a discharge of the overcharged capacitor. It is possible to think of the MOSFET as voltage dependent resistors, which leads to improved balancing times compared to passive resistors.

### 4.4 Active Balancing with Operational Amplifier

Any application that needs a shorter balancing time will have to apply an active balancing. Active balancing always involves integrated circuits such as operational amplifier (OP-AMP), which is illustrated in Figure 5. The circuit contains red and green arrows, which represent the corresponding physical current flow for the case where  $C_1$  has either over ( $+\Delta V$ ) or under voltage ( $-\Delta V$ ).

 

**Figure 5: Circuit for active balancing with feedback amplifier.**

The balancing resistance, as used for the active balancing, is determined on the basis of the designated internal resistance of the OP-AMP, which is at least the order of  $10\text{ M}\Omega$  but usually even higher. To ensure the voltage detection at the inputs the balancing resistances  $R_{B,1}$  and  $R_{B,2}$  should be about 10 times smaller than the internal resistance of the OP-AMP. As a result, the loss through the balancing resistance can be as small as for the internal resistance of the SC.


However, a more significant cause of loss is the supply current, delivered through contacts  $V_+$  and  $V_-$ . Depending on the type of OP-AMP the permeant supply current may be in the range from  $1\ \mu\text{A}$  to  $10\ \text{mA}$ . This may pose a technical obstacle, that needs to be considered at the conceptual design-in phase.

The balancing current is provided by the output of the OP-AMP and regulated via the feedback loop. The damping resistance  $R_D$  at the output

of the OP-AMP is only as high as to prevent oscillation during the current regulation.

### 4.5 Active Balancing with DC-DC converter

Another concept of active charge equalization consists of DC-DC converters, each connected across two neighboring cells, as illustrated in Figure 6. Due to the low losses of commercially available converters, this concept is in terms of balancing time and power burn more efficient than passive balancing.

 

**Figure 6: Schematic balancing circuit with DC-DC Conversion.**

There are balanced buck-boost SC chargers available on the market, which are suitable for a range of applications. Available for instance are the

- LTC3351, Hot Swappable Backup Supercapacitor Charger

or the

- LTC3128, Supercapacitor Charger and Balancer

from Analog Devices. Additional information are also provided in the Würth Elektronik (WE) Webinar [“WE Backup Your Application – A real life SC backup solution”](#).<sup>[11]</sup>

Although DC-DC converters constitute a relatively costly balancing strategy, they are on the other side also an elaborate and comprehensive solution. They may provide complete charging and hot swappable charging solutions with low power consumption. The choice at the end is always with the developer.

## 5 Measurements

The voltage measurements were performed with a self-developed measurement setup, based on the integrated circuit CY8CKIT-059 from PSoC. The data acquisition was utilized with an Excel-script. The measurement setup including the programming of the script were developed by Jon-Izkue Rodriguez from WE eiSos.

The power supply we used was the HMP4040 from Rohde & Schwarz. The currents for the determination of the power dissipation were measured with M252A METRAHit ESPECIAL Current Transformer Connection Multimeter from Gossen-Metrawatt.











# Application Note

## Keep the Balance – Balancing of Supercapacitors



We also derived formulas for the:

- calculation of the charging voltages in a disbalanced system

$$V_1 = \frac{V_g}{\left(\frac{C_1}{C_2} + 1\right)}$$

and

$$V_2 = \frac{V_g}{\left(\frac{C_2}{C_1} + 1\right)}$$

- required balancing current

$$I = 2 \cdot \frac{\Delta V}{\Delta t} \cdot C_r$$

- resistor balancing time

$$t_b = 3 \cdot R_b \cdot C_r$$

- balancing time for balancing with Zener diodes

$$t_b^* = 3 \cdot \left( \frac{V_r^2}{f \cdot P_r} \cdot C_r \right)$$

- half-life self-discharge time

$$t_{\text{loss}} = 0.7 \cdot \left( \frac{V_g}{I_{\text{loss}}} \cdot C_{\text{stack}} \right)$$

- theoretical half-life self-discharge time for a stack, balanced with a Zener diode

$$t_{\text{loss}}^* = 0.7 \cdot \left( \frac{V_g}{f \cdot I_{\text{loss}}} \cdot C_{\text{stack}} \right)$$

We hope the measurement examples illustrated the general advantages and disadvantages of each approach.

# Application Note

## Keep the Balance – Balancing of Supercapacitors



### A Appendix

#### A.1 Conservation of Charge and Disbalance

In a series connection of N capacitors with capacitance  $C_N$  the total capacitance is

$$\frac{1}{C_g} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}$$

with  $C_g$  as effective (or gross) capacitance. It is a physical requirement that in a series connection the amount of charges  $q$ , stored on each capacitor, is equal, thus

$$q = q_1 = q_2 = \dots = q_N.$$

With Kirchhoff's voltage law

$$V_g = V_1 + V_2 + \dots + V_N$$

we arrive at a relation between the total applied voltage, capacitance and charge

$$V_g = \frac{q}{C_g} = \frac{q}{C_1} + \frac{q}{C_2} + \dots + \frac{q}{C_N}$$

Remark: In principle any stack can be equivalently modeled as a stack of two capacitors (with its corresponding voltage division):

$$\frac{1}{C_g} = \frac{1}{C_1} + \underbrace{\left( \frac{1}{C_2} + \dots + \frac{1}{C_N} \right)}_{= C_2'}$$

For the sake of simplicity, we continue with a system of two equally rated capacitors  $C_1$  and  $C_2$ :

$$V_g = V_1 + V_2$$

$$V_2 = \frac{q}{C_2}$$

and

$$V_1 = \frac{q}{C_1}$$

$$\frac{V_2}{V_1} = \frac{C_1}{C_2}$$

$$V_g = V_1 + \frac{C_1}{C_2} \cdot V_1 = \left( \frac{C_1}{C_2} + 1 \right) \cdot V_1$$

$$V_1 = \frac{V_g}{\left( \frac{C_1}{C_2} + 1 \right)}$$

$$\frac{V_1}{V_2} = \frac{C_2}{C_1}$$

$$V_g = \frac{C_2}{C_1} \cdot V_2 + V_2 = \left( \frac{C_2}{C_1} + 1 \right) \cdot V_2$$

$$V_2 = \frac{V_g}{\left( \frac{C_2}{C_1} + 1 \right)}$$

Above we have calculated the absolute voltage level  $V_1$  and  $V_2$  of capacitor 1 and capacitor 2, respectively.

In the following we use these expressions to calculate actual magnitude of the disbalance  $\Delta V$  assuming the capacitor stack is balanced at

$$\frac{V_g}{2}$$

We may at first consider the voltage  $V_1$  at capacitor 1

$$\Delta V_1 = \frac{V_g}{2} - \frac{V_g}{\left( \frac{C_1}{C_2} + 1 \right)} = \frac{V_g \left( \frac{C_1}{C_2} + 1 \right) - 2 \cdot V_g}{2 \left( \frac{C_1}{C_2} + 1 \right)}$$

$$\Delta V_1 = \frac{V_g \left( \frac{C_1}{C_2} + 1 - 2 \right)}{2 \left( \frac{C_1}{C_2} + 1 \right)} = \frac{V_g}{2} \cdot \frac{\frac{C_1}{C_2} - 1}{\frac{C_1}{C_2} + 1}$$

$$\Delta V_1 = \frac{V_g}{2} \cdot \frac{\frac{C_1}{C_2} - \frac{C_2}{C_2}}{\frac{C_1}{C_2} + \frac{C_2}{C_2}}$$

$$\Delta V_1 = \frac{V_g}{2} \cdot \frac{\frac{C_1}{C_2} - \frac{C_2}{C_2}}{\frac{C_1}{C_2} + \frac{C_2}{C_2}} = \frac{V_g}{2} \cdot \frac{C_2 (C_1 - C_2)}{C_2 (C_1 + C_2)}$$

$$\Delta V_1 = \frac{V_g}{2} \cdot \frac{(C_1 - C_2)}{(C_1 + C_2)}$$

Similarly we arrive for  $V_2$  at

$$\Delta V_2 = - \frac{V_g}{2} \cdot \frac{(C_1 - C_2)}{(C_1 + C_2)}$$

Hence, the magnitude of the disbalance at each capacitor is equal:


$$\Delta V = |\Delta V_1| = |\Delta V_2| = \left| \frac{V_g}{2} \cdot \frac{(C_1 - C_2)}{(C_1 + C_2)} \right|$$

# Application Note

## Keep the Balance – Balancing of Supercapacitors



### A.2 Disbalance Voltage Level

 

**Figure 18: Voltage levels of a capacitor with imbalance  $\Delta V$ .**

As addressed above, charging two series-connected ideal capacitors with two different capacitances results in an unevenly distributed voltage, which results in a disbalance  $\Delta V$ . Figure 18 shows the voltage levels of a capacitor relative to its nominal voltage  $V_r$ . Due to the disbalance  $\Delta V$ , a capacitor has an initial state of charge  $V_i$ , which occurs after the capacitor is fully charged. Due to balancing, the capacitor reaches the actual state of charge  $V_c$  with respect to ground ( $V_0$ ), which can also be specified with respect to  $V_i$ :

$$V_c^* = V_c - V_i.$$

Two ratios may now be considered:

$$p^* = \frac{V_c^*}{\Delta V} = \frac{(V_c - V_i)}{\Delta V} \quad (I)$$

As well as

$$p = \frac{V_c}{V_r} \quad (II)$$

The ratio  $p^*$  describes the charging state in relation to the disbalance  $\Delta V$  and  $p$  the charging state in relation to the rated voltage  $V_r$ . The balancing time in this R-C system, with  $R_b$  as equivalent series resistance and  $C$  as capacitance, is calculated with

$$\ln\left(\frac{1}{1 - p^*}\right) \cdot (R_b \cdot C)$$

However,  $p^*$  does not explicitly contain the absolute value  $V_r$ . In order to find such a relation  $p$  and  $p^*$  shall be rewritten

$$p^* + \frac{V_i}{\Delta V} = \frac{V_c}{\Delta V}$$

$$p^* \Delta V + V_i = V_c \quad (I')$$

Substituting I' in II yields:

$$p = \frac{V_c}{V_r} = \frac{p^* \Delta V + V_i}{V_r} \quad (II')$$

With  $\Delta V = V_r - V_i$  equation II' may also be rewritten as

$$p = \frac{p^* (V_r - V_i) + V_i}{V_r}$$

$$p = \frac{p^* \Delta V + V_r - \Delta V}{V_r}$$

or

$$p^* = \frac{pV_r - V_r + \Delta V}{\Delta V} = \frac{V_r (p - 1) + \Delta V}{\Delta V}$$

With  $p = 0.9999$  (99.99 %) and the theoretically maximum possible disbalance of  $\Delta V = 0.49$  V ( $C_{tol.} = -10\%/+30\%$ ) it can be calculated that

$$p^* = \frac{2.7 \text{ V} (0.9999 - 1) + 0.49 \text{ V}}{0.49}$$

$$p^* = 0.99945 \text{ (99.945 \%)}$$

With the value of  $p^*$  the respective balancing time may now be calculated with  $t_b = f (R_b C)$ , where

$$f = \ln\left(\frac{1}{1 - p^*}\right)$$

The below Table 3 provides a summary of calculations of  $p^*$  and  $f$  for different parameters

p	$\Delta V$ [V] (C tol. [%])	$p^*$	f
<b>0.9999</b>	0.49 - 10%/30%	0.99945	7.5
<b>0.999</b>	0.49 - 10%/30%	0.9945	5.2
<b>0.995</b>	0.49 - 10%/30%	0.9725	3.6
<b>0.9999</b>	0.27 ± 10%	0.999	6.9
<b>0.999</b>	0.27 ± 10%	0.99	4.6
<b>0.995</b>	0.27 ± 10%	0.95	3.0

**Table 3: Calculation of  $p^*$  and  $f$  for different parameters.**

# Application Note

## Keep the Balance – Balancing of Supercapacitors



### A.3 Literature

- [1] F. Beguin und E. Frackowiak (Hrsg.), Supercapacitors Materials, Systems, and Applications, WILEY-VCH Verlag, ISBN: 978-3-527-32883-3, S. 352ff (2013)
- [2] R. Kötz et al., Principles and applications of electrochemical capacitors, *Electrochimica Acta*, 45 (15-16), 2483-2498, doi: 10.1016/s0013-4686(00)00354-6 (2000)
- [3] D. Linzen et al., Analysis and Evaluation of Charge-Balancing Circuits on Performance, Reliability, and Lifetime, of Supercapacitor Systems. *IEEE-Transactions on Industry Applications*, 41(5), 1135-1141, doi: 10.1109/tia.2005.853375 (2005).
- [4] H. Li et al., Synchronized Cell-Balancing Charging of Supercapacitors. *IFAC-PapersOnLine*, 50(1), 3338–3343, doi:10.1016/j.ifacol.2017.08.518 (2017)
- [5] R. Kalbitz et al., Supercapacitor – A Guide for the Design-In Process, Application Note ANP077, WE eiSos (2020)
- [6] Y. Qu et al., Overview of supercapacitor cell voltage balancing methods for an electric vehicle, 2013 IEEE ECCE Asia Downunder, doi: 10.1109/ecce-asia.2013.6579196 (2013)
- [7] F. M. Ibanez, Analyzing the Need for a Balancing System in Supercapacitor Energy Storage Systems, *IEEE Transactions on Power Electronics*, 33(3), 2162-2171, doi: 10.1109/TPEL.2017.2697406 (2018)
- [8] B.T. Prashant Sing et al., Extensive review on Supercapacitor cell voltage balancing. *E3S Web of Conferences*. 87. 01010. 10.1051/e3sconf/20198701010 (2019)
- [9] K. B. McAfee et al., Observations of Zener Current in Germanium-p-n Junctions, *Physical Review*, 83(3), 650–651. doi:10.1103/physrev.83.650 (1951)
- [10] [Link to Supercapacitor Modul in REDEXPERT](#)
- [11] [Link to Online-Seminar "WE Backup Your Application – A real life Supercapacitor backup solution"](#)

# Application Note

## Keep the Balance – Balancing of Supercapacitors



### IMPORTANT NOTICE

The Application Note is based on our knowledge and experience of typical requirements concerning these areas. It serves as general guidance and should not be construed as a commitment for the suitability for customer applications by Würth Elektronik eiSos GmbH & Co. KG. The information in the Application Note is subject to change without notice. This document and parts thereof must not be reproduced or copied without written permission, and contents thereof must not be imparted to a third party nor be used for any unauthorized purpose.

Würth Elektronik eiSos GmbH & Co. KG and its subsidiaries and affiliates (WE) are not liable for application assistance of any kind. Customers may use WE's assistance and product recommendations for their applications and design. The responsibility for the applicability and use of WE Products in a particular customer design is always solely within the authority of the customer. Due to this fact it is up to the customer to evaluate and investigate, where appropriate, and decide whether the device with the specific product characteristics described in the product specification is valid and suitable for the respective customer application or not.

The technical specifications are stated in the current data sheet of the products. Therefore the customers shall use the data sheets and are cautioned to verify that data sheets are current. The current data sheets can be downloaded at [www.we-online.com](http://www.we-online.com). Customers shall strictly observe any product-specific notes, cautions and warnings. WE reserves the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services.

WE DOES NOT WARRANT OR REPRESENT THAT ANY LICENSE, EITHER EXPRESS OR IMPLIED, IS GRANTED UNDER ANY PATENT RIGHT,

COPYRIGHT, MASK WORK RIGHT, OR OTHER INTELLECTUAL PROPERTY RIGHT RELATING TO ANY COMBINATION, MACHINE, OR PROCESS IN WHICH WE PRODUCTS OR SERVICES ARE USED. INFORMATION PUBLISHED BY WE REGARDING THIRD-PARTY PRODUCTS OR SERVICES DOES NOT CONSTITUTE A LICENSE FROM WE TO USE SUCH PRODUCTS OR SERVICES OR A WARRANTY OR ENDORSEMENT THEREOF.

WE products are not authorized for use in safety-critical applications, or where a failure of the product is reasonably expected to cause severe personal injury or death. Moreover, WE products are neither designed nor intended for use in areas such as military, aerospace, aviation, nuclear control, submarine, transportation (automotive control, train control, ship control), transportation signal, disaster prevention, medical, public information network etc. Customers shall inform WE about the intent of such usage before design-in stage. In certain customer applications requiring a very high level of safety and in which the malfunction or failure of an electronic component could endanger human life or health, customers must ensure that they have all necessary expertise in the safety and regulatory ramifications of their applications. Customers acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of WE products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by WE.

CUSTOMERS SHALL INDEMNIFY WE AGAINST ANY DAMAGES ARISING OUT OF THE USE OF WE PRODUCTS IN SUCH SAFETY-CRITICAL APPLICATIONS.

### USEFUL LINKS



Application Notes

[www.we-online.com/app-notes](http://www.we-online.com/app-notes)



**REDEXPERT** Design Tool

[www.we-online.com/redexpert](http://www.we-online.com/redexpert)



Toolbox

[www.we-online.com/toolbox](http://www.we-online.com/toolbox)



Product catalog

[www.we-online.com/products](http://www.we-online.com/products)

### CONTACT INFORMATION

[appnotes@we-online.com](mailto:appnotes@we-online.com)

Tel. +49 7942 945 - 0



Würth Elektronik eiSos GmbH & Co. KG  
Max-Eyth-Str. 1 · 74638 Waldenburg · Germany

[www.we-online.com](http://www.we-online.com)

